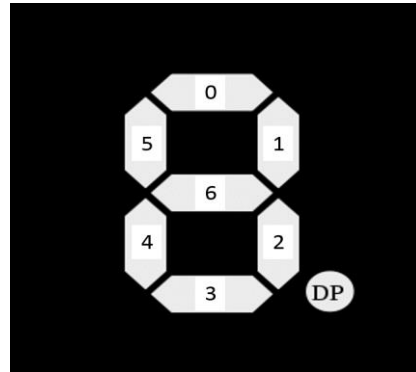


### Truth Table Conversion (Binary -> Digit)

Binary	Digit
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	*
1011	*
1100	*
1101	*
1110	*
1111	*


don't  
care

### Seven Segment Display Numbering



### Another Example of the Digit "5", Drive Segments 1,4 high "1" to display digit "5"

	Digit 5
segment[0]	
segment[1]	1
segment[2]	
segment[3]	
segment[4]	1
segment[5]	
segment[6]	

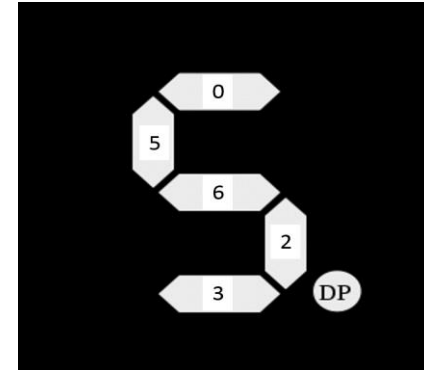

### Map of What Segments to Drive for Each Digit

	Digit 0	Digit 1	Digit 2	Digit 3	Digit 4	Digit 5	Digit 6	Digit 7	Digit 8	Digit 9
segment[0]		1			1					
segment[1]						1	1			
segment[2]			1							
segment[3]		1			1			1		1
segment[4]		1		1	1	1		1		1
segment[5]		1	1	1				1		
segment[6]	1	1						1		

\*note, on Altera Seven Segment Displays, they are common cathode, thus driving a segment to "1" will turn it off, and driving it to "0" will turn it on

\*\*note, only added high "1" values for ease of reading, didn't add low "0" values, but you will have to do this in your verilog code.

### Example of Segment 1, and when it needs to be high "1" to display all of the digits (0-9)

	Digit 0	Digit 1	Digit 2	Digit 3	Digit 4	Digit 5	Digit 6	Digit 7	Digit 8	Digit 9
segment[1]						1	1			

	Digit 5	Digit 6
segment[1]	1	1

```
assign segment[1] = (~C[3]&C[2]&~C[1]&C[0])|(~C[3]&C[2]&C[1]&~C[0]);
//0101 OR 0110
```